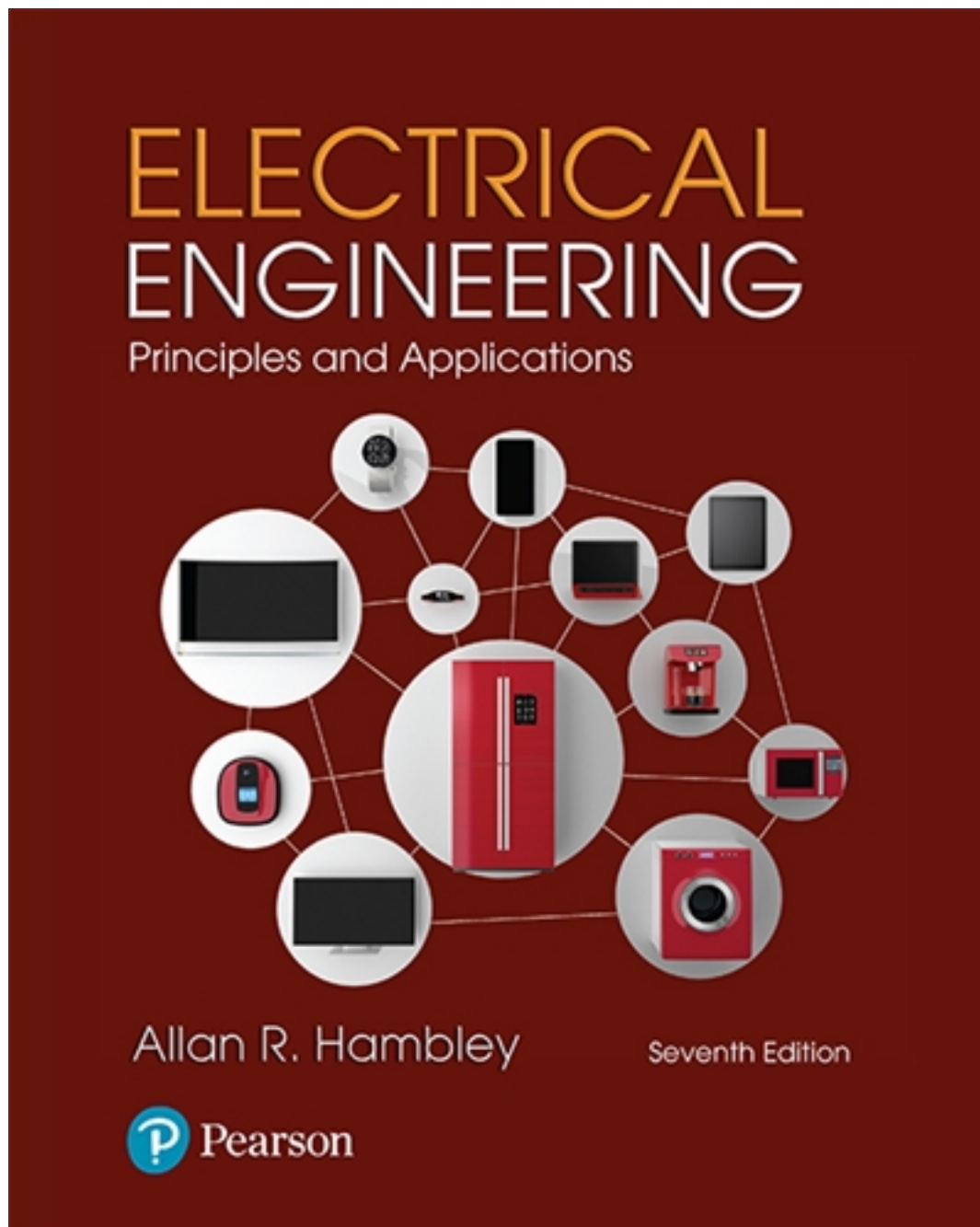


Solutions for Electrical Engineering 7th Edition by Hambley

[CLICK HERE TO ACCESS COMPLETE Solutions](#)



Solutions

CHAPTER 1

Exercises

E1.1 Charge = Current $\times$ Time = (2 A) $\times$ (10 s) = 20 C

E1.2 $i(t) = \frac{dq(t)}{dt} = \frac{d}{dt}(0.01\sin(200t)) = 0.01 \times 200\cos(200t) = 2\cos(200t) \text{ A}$

E1.3 Because i_2 has a positive value, positive charge moves in the same direction as the reference. Thus, positive charge moves downward in element C.

Because i_3 has a negative value, positive charge moves in the opposite direction to the reference. Thus positive charge moves upward in element E.

E1.4 Energy = Charge $\times$ Voltage = (2 C) $\times$ (20 V) = 40 J

Because v_{ab} is positive, the positive terminal is a and the negative terminal is b . Thus the charge moves from the negative terminal to the positive terminal, and energy is removed from the circuit element.

E1.5 i_{ab} enters terminal a . Furthermore, v_{ab} is positive at terminal a . Thus the current enters the positive reference, and we have the passive reference configuration.

E1.6 (a) $p_a(t) = v_a(t)i_a(t) = 20t^2$

$$w_a = \int_0^{10} p_a(t) dt = \int_0^{10} 20t^2 dt = \left. \frac{20t^3}{3} \right|_0^{10} = \frac{20t^3}{3} = 6667 \text{ J}$$

(b) Notice that the references are opposite to the passive sign convention. Thus we have:

$$p_b(t) = -v_b(t)i_b(t) = 20t - 200$$

$$w_b = \int_0^{10} p_b(t) dt = \int_0^{10} (20t - 200) dt = 10t^2 - 200t \Big|_0^{10} = -1000 \text{ J}$$

E1.7 (a) Sum of currents leaving = Sum of currents entering
 $i_a = 1 + 3 = 4 \text{ A}$

(b) $2 = 1 + 3 + i_b \Rightarrow i_b = -2 \text{ A}$

(c) $0 = 1 + i_c + 4 + 3 \Rightarrow i_c = -8 \text{ A}$

E1.8 Elements A and B are in series. Also, elements E , F , and G are in series.

E1.9 Go clockwise around the loop consisting of elements A , B , and C :
 $-3 - 5 + v_c = 0 \Rightarrow v_c = 8 \text{ V}$

Then go clockwise around the loop composed of elements C , D and E :
 $-v_c - (-10) + v_e = 0 \Rightarrow v_e = -2 \text{ V}$

E1.10 Elements E and F are in parallel; elements A and B are in series.

E1.11 The resistance of a wire is given by $R = \frac{\rho L}{A}$. Using $A = \pi d^2 / 4$ and substituting values, we have:

$$9.6 = \frac{1.12 \times 10^{-6} \times L}{\pi(1.6 \times 10^{-3})^2 / 4} \Rightarrow L = 17.2 \text{ m}$$

E1.12 $P = V^2 / R \Rightarrow R = V^2 / P = 144 \Omega \Rightarrow I = V / R = 120 / 144 = 0.833 \text{ A}$

E1.13 $P = V^2 / R \Rightarrow V = \sqrt{PR} = \sqrt{0.25 \times 1000} = 15.8 \text{ V}$
 $I = V / R = 15.8 / 1000 = 15.8 \text{ mA}$

E1.14 Using KCL at the top node of the circuit, we have $i_1 = i_2$. Then, using KVL going clockwise, we have $-v_1 - v_2 = 0$; but $v_1 = 25 \text{ V}$, so we have $v_2 = -25 \text{ V}$. Next we have $i_1 = i_2 = v_2 / R = -1 \text{ A}$. Finally, we have $P_R = v_2 i_2 = (-25) \times (-1) = 25 \text{ W}$ and $P_s = v_1 i_1 = (25) \times (-1) = -25 \text{ W}$.

E1.15 At the top node we have $i_R = i_s = 2 \text{ A}$. By Ohm's law we have $v_R = Ri_R = 80 \text{ V}$. By KVL we have $v_s = v_R = 80 \text{ V}$. Then $p_s = -v_s i_s = -160 \text{ W}$ (the minus sign is due to the fact that the references for v_s and i_s are opposite to the passive sign configuration). Also we have $P_R = v_R i_R = 160 \text{ W}$.

Problems

- P1.1** Broadly, the two objectives of electrical systems are:
1. To gather, store, process, transport and present information.
 2. To distribute, store, and convert energy between various forms.
- P1.2** Four reasons that non-electrical engineering majors need to learn the fundamentals of EE are:
1. To pass the Fundamentals of Engineering Exam.
 2. To be able to lead in the design of systems that contain electrical/electronic elements.
 3. To be able to operate and maintain systems that contain electrical/electronic functional blocks.
 4. To be able to communicate effectively with electrical engineers.
- P1.3** Eight subdivisions of EE are:
1. Communication systems.
 2. Computer systems.
 3. Control systems.
 4. Electromagnetics.
 5. Electronics.
 6. Photonics.
 7. Power systems.
 8. Signal Processing.
- P1.4** Responses to this question are varied.
- P1.5** (a) Electrical current is the time rate of flow of net charge through a conductor or circuit element. Its units are amperes, which are equivalent to coulombs per second.
- (b) The voltage between two points in a circuit is the amount of energy transferred per unit of charge moving between the points. Voltage has units of volts, which are equivalent to joules per coulomb.

(c) The current through an open switch is zero. The voltage across the switch can be any value depending on the circuit.

(d) The voltage across a closed switch is zero. The current through the switch can be any value depending of the circuit.

(e) Direct current is constant in magnitude and direction with respect to time.

(f) Alternating current varies either in magnitude or direction with time.

- P1.6**
- (a) A conductor is analogous to a frictionless pipe.
 - (b) An open switch is analogous to a closed valve.
 - (c) A resistance is analogous to a constriction in a pipe or to a pipe with friction.
 - (d) A battery is analogous to a pump.

P1.7 Electrons per second = $\frac{1 \text{ coulomb/s}}{1.60 \times 10^{-19} \text{ coulomb/electron}} = 6.25 \times 10^{18}$

- P1.8*** The reference direction for i_{ab} points from a to b . Because i_{ab} has a negative value, the current is equivalent to positive charge moving opposite to the reference direction. Finally since electrons have negative charge, they are moving in the reference direction (i.e., from a to b).

For a constant (dc) current, charge equals current times the time interval. Thus, $Q = (5 \text{ A}) \times (3 \text{ s}) = 15 \text{ C}$.


- P1.9** The positive reference for v is at the head of the arrow, which is terminal a . The positive reference for v_{ba} is terminal b . Thus, we have $v_{ba} = -v = -12 \text{ V}$. Also, i is the current entering terminal a , and i_{ba} is the current leaving terminal a . Thus, we have $i = -i_{ba} = 2 \text{ A}$. Thus, current enters the positive reference and energy is being delivered to the device.

- P1.10** To stop current flow, we break contact between the conducting parts of the switch, and we say that the switch is open. The corresponding fluid

analogy is a valve that does not allow fluid to pass through. This corresponds to a closed valve. Thus, a closed valve is analogous to an open switch.

$$\text{P1.11*} \quad i(t) = \frac{dq(t)}{dt} = \frac{d}{dt}(2 + 3t) = 3 \text{ A}$$

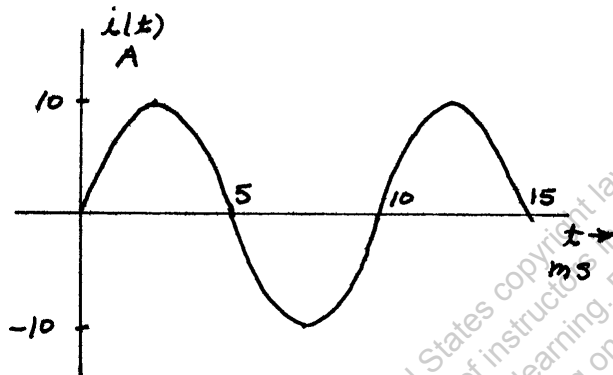P1.12 (a) The sine function completes one cycle for each 2π radian increase in the angle. Because the angle is $200\pi t$, one cycle is completed for each time interval of 0.01 s. The sketch is:



$$\begin{aligned} \text{(b)} \quad Q &= \int_0^{0.005} i(t) dt = \int_0^{0.005} 10 \sin(200\pi t) dt = (10 / 200\pi) \cos(200\pi t) \Big|_0^{0.005} \\ &= 0.0318 \text{ C} \end{aligned}$$

$$\begin{aligned} \text{(c)} \quad Q &= \int_0^{0.01} i(t) dt = \int_0^{0.01} 10 \sin(200\pi t) dt = (10 / 200\pi) \cos(200\pi t) \Big|_0^{0.01} \\ &= 0 \text{ C} \end{aligned}$$

$$\text{P1.13*} \quad Q = \int_0^{\infty} i(t) dt = \int_0^{\infty} 2e^{-t} dt = -2e^{-t} \Big|_0^{\infty} = 2 \text{ coulombs}$$

$$\text{P1.14} \quad i(t) = \frac{dq(t)}{dt} = \frac{d}{dt}(3 - 3e^{-2t}) = 6e^{-2t} \text{ A}$$

P1.15 The number of electrons passing through a cross section of the wire per second is

$$N = \frac{15}{1.6 \times 10^{-19}} = 9.375 \times 10^{19} \text{ electrons/second}$$

The volume of copper containing this number of electrons is

$$\text{volume} = \frac{9.375 \times 10^{19}}{10^{29}} = 9.375 \times 10^{-10} \text{ m}^3$$

The cross sectional area of the wire is

$$A = \frac{\pi d^2}{4} = 3.301 \times 10^{-6} \text{ m}^2$$

Finally, the average velocity of the electrons is

$$u = \frac{\text{volume}}{A} = 0.2840 \text{ mm/s}$$

P1.16* The charge flowing through the battery is

$$Q = (5 \text{ amperes}) \times (24 \times 3600 \text{ seconds}) = 432 \times 10^3 \text{ coulombs}$$

and the stored energy is

$$\text{Energy} = QV = (432 \times 10^3) \times (12) = 5.184 \times 10^6 \text{ joules}$$

(a) Equating gravitational potential energy, which is mass times height times the acceleration due to gravity, to the energy stored in the battery and solving for the height, we have

$$h = \frac{\text{Energy}}{mg} = \frac{5.184 \times 10^6}{30 \times 9.8} = 17.6 \text{ km}$$

(b) Equating kinetic energy to stored energy and solving for velocity, we have

$$v = \sqrt{\frac{2 \times \text{Energy}}{m}} = 587.9 \text{ m/s}$$

(c) The energy density of the battery is

$$\frac{5.184 \times 10^6}{30} = 172.8 \times 10^3 \text{ J/kg}$$

which is about 0.384% of the energy density of gasoline.

P1.17 $Q = \text{current} \times \text{time} = (2 \text{ amperes}) \times (20 \text{ seconds}) = 40 \text{ coulombs}$

$$\text{Energy} = QV = (20) \times (10) = 200 \text{ joules}$$

Because i_{ba} is positive, if the current were carried by positive charge it would be entering terminal b . Electrons enter terminal a . The energy is taken from the element.

P1.18 The electron gains $1.6 \times 10^{-19} \times 9 = 14.4 \times 10^{-19}$ joules

P1.19* $Q = \text{current} \times \text{time} = (5 \text{ amperes}) \times (36,000 \text{ seconds}) = 1.8 \times 10^5$ coulombs

$$\text{Energy} = QV = (1.8 \times 10^5) \times (12) = 2.16 \times 10^6 \text{ joules}$$

P1.20 If the current is referenced to flow into the positive reference for the voltage, we say that we have the passive reference configuration. Using double subscript notation, if the order of the subscripts are the same for the current and voltage, we have a passive reference configuration.

P1.21* (a) $P = -v_a i_a = 30 \text{ W}$ Energy is being absorbed by the element.

(b) $P = v_b i_b = 30 \text{ W}$ Energy is being absorbed by the element.

(c) $P = -v_{DE} i_{ED} = -60 \text{ W}$ Energy is being supplied by the element.

P1.22 The amount of energy is $W = QV = (3 \text{ C}) \times (10 \text{ V}) = 30 \text{ J}$. Because the reference polarity is positive at terminal a and the voltage value is negative, terminal b is actually the positive terminal. Because the charge moves from the negative terminal to the positive terminal, energy is removed from the device.

P1.23* $Q = w/V = (600 \text{ J})/(12 \text{ V}) = 50 \text{ C}$.


To increase the chemical energy stored in the battery, positive charge should move from the positive terminal to the negative terminal, in other words from a to b . Electrons move from b to a .

P1.24 $p(t) = v(t)i(t) = 20e^{-t} \text{ W}$

$$\text{Energy} = \int_0^{\infty} p(t) dt = -20e^{-t} \Big|_0^{\infty} = 20 \text{ joules}$$

The element absorbs the energy.

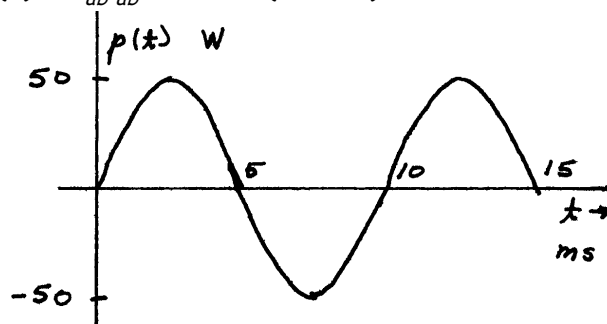P1.25 (a) $p(t) = v_{ab} i_{ab} = 50 \sin(200\pi t) \text{ W}$



(b) $w = \int_0^{0.005} p(t) dt = \int_0^{0.005} 50 \sin(200\pi t) dt = (50 / 200\pi) \cos(200\pi t) \Big|_0^{0.005}$
 $= 0.1592 \text{ J}$

(c) $w = \int_0^{0.01} p(t) dt = \int_0^{0.01} 50 \sin(200\pi t) dt = (50 / 200\pi) \cos(200\pi t) \Big|_0^{0.01}$
 $= 0 \text{ J}$

P1.26* $\text{Energy} = \frac{\text{Cost}}{\text{Rate}} = \frac{\$60}{0.12 \text{ \$/kWh}} = 500 \text{ kWh}$

$P = \frac{\text{Energy}}{\text{Time}} = \frac{500 \text{ kWh}}{30 \times 24 \text{ h}} = 694.4 \text{ W}$ $I = \frac{P}{V} = \frac{694.4}{120} = 5.787 \text{ A}$

$\text{Reduction} = \frac{60}{694.4} \times 100\% = 8.64\%$


- P1.27** (a) $P = 60 \text{ W}$ delivered to element A.
 (b) $P = 60 \text{ W}$ taken from element A.
 (c) $P = 60 \text{ W}$ delivered to element A.

- P1.28*** (a) $P = 60 \text{ W}$ taken from element A.
 (b) $P = 60 \text{ W}$ delivered to element A.
 (c) $P = 60 \text{ W}$ taken from element A.

P1.29 The power that can be delivered by the cell is $p = vi = 0.12 \text{ W}$. In 75 hours, the energy delivered is $W = pT = 9 \text{ Whr} = 0.009 \text{ kWhr}$. Thus the unit cost of the energy is $\text{Cost} = (0.50) / (0.009) = 55.56 \text{ \$/kWhr}$ which is 463 times the typical cost of energy from electric utilities.

P1.30 The current supplied to the electronics is $i = p/v = 50/12.6 = 3.968$ A. The ampere-hour rating of the battery is the operating time to discharge the battery multiplied by the current. Thus, the operating time is $T = 100/i = 25.2$ hours. The energy delivered by the battery is $W = pT = 50(25.2) = 1260$ wh = 1.26 kWh. Neglecting the cost of recharging, the cost of energy for 300 discharge cycles is $Cost = 75/(300 \times 1.26) = 0.1984$ \$/kWh.

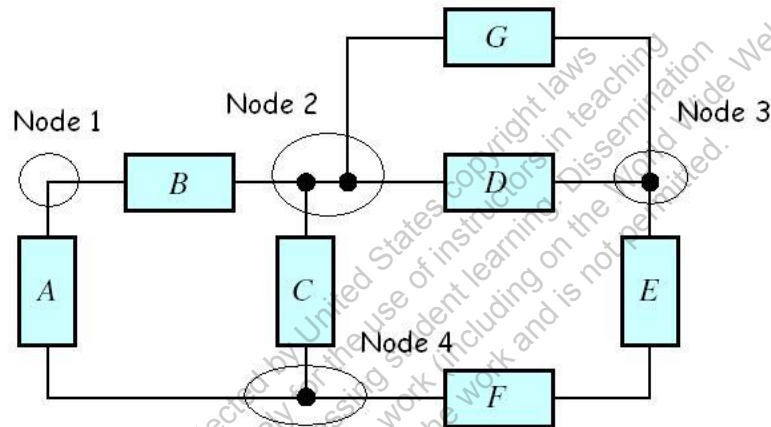P1.31 A node is a point that joins two or more circuit elements. All points joined by ideal conductors are electrically equivalent. Thus, there are four nodes in the circuit at hand:



P1.32 The sum of the currents entering a node equals the sum of the currents leaving.

P1.33 The currents in series-connected elements are equal.

P1.34 For a proper fluid analogy to electric circuits, the fluid must be incompressible. Otherwise the fluid flow rate out of an element could be more or less than the inward flow. Similarly the pipes must be inelastic so the flow rate is the same at all points along each pipe.

P1.35* Elements A and B are in series. Also, elements E and F are in series.

- P1.36** (a) Elements C and D are in series.
 (b) Because elements C and D are in series, the currents are equal in magnitude. However, because the reference directions are opposite, the algebraic signs of the current values are opposite. Thus, we have $i_c = -i_d$.
 (c) At the node joining elements A , B , and C , we can write the KCL equation $i_b = i_a + i_c = 3 + 1 = 4 \text{ A}$. Also we found earlier that $i_d = -i_c = -1 \text{ A}$.

- P1.37*** At the node joining elements A and B , we have $i_a + i_b = 0$. Thus, $i_a = -2 \text{ A}$. For the node at the top end of element C , we have $i_b + i_c = 3$. Thus, $i_c = 1 \text{ A}$. Finally, at the top right-hand corner node, we have $3 + i_e = i_d$. Thus, $i_d = 4 \text{ A}$. Elements A and B are in series.

- P1.38*** We are given $i_a = 2 \text{ A}$, $i_b = 3 \text{ A}$, $i_d = -5 \text{ A}$, and $i_h = 4 \text{ A}$. Applying KCL, we find

$$\begin{aligned} i_c &= i_b - i_a = 1 \text{ A} & i_e &= i_c + i_h = 5 \text{ A} \\ i_f &= i_a + i_d = -3 \text{ A} & i_g &= i_f - i_h = -7 \text{ A} \end{aligned}$$

- P1.39** We are given $i_a = -1 \text{ A}$, $i_c = 3 \text{ A}$, $i_g = 5 \text{ A}$, and $i_h = 1 \text{ A}$. Applying KCL, we find

$$\begin{aligned} i_b &= i_c + i_a = 2 \text{ A} & i_e &= i_c + i_h = 4 \text{ A} \\ i_d &= i_f - i_a = 7 \text{ A} & i_f &= i_g + i_h = 6 \text{ A} \end{aligned}$$

- P1.40** If one travels around a closed path adding the voltages for which one enters the positive reference and subtracting the voltages for which one enters the negative reference, the total is zero.

- P1.41** (a) Elements A and B are in parallel.
 (b) Because elements A and B are in parallel, the voltages are equal in magnitude. However because the reference polarities are opposite, the algebraic signs of the voltage values are opposite. Thus, we have $v_a = -v_b$.
 (c) Writing a KVL equation while going clockwise around the loop composed of elements A , C and D , we obtain $v_a - v_d - v_c = 0$. Solving for v_c and substituting values, we find $v_c = 7 \text{ V}$. Also we have $v_b = -v_a = -2 \text{ V}$.

P1.42* Summing voltages for the lower left-hand loop, we have $-5 + v_a + 10 = 0$, which yields $v_a = -5$ V. Then for the top-most loop, we have $v_c - 15 - v_a = 0$, which yields $v_c = 10$ V. Finally, writing KCL around the outside loop, we have $-5 + v_c + v_b = 0$, which yields $v_b = -5$ V.

P1.43 We are given $v_a = 5$ V, $v_b = 7$ V, $v_f = -10$ V, and $v_h = 6$ V. Applying KVL, we find

$$\begin{aligned} v_d &= v_a + v_b = 12 \text{ V} & v_c &= -v_a - v_f - v_h = -1 \text{ V} \\ v_e &= -v_a - v_c + v_d = 8 \text{ V} & v_g &= v_e - v_h = 2 \text{ V} \\ v_b &= v_c + v_e = 7 \text{ V} \end{aligned}$$

P1.44* Applying KCL and KVL, we have

$$\begin{aligned} i_c &= i_a - i_d = 1 \text{ A} & i_b &= -i_a = -2 \text{ A} \\ v_b &= v_d - v_a = -6 \text{ V} & v_c &= v_d = 4 \text{ V} \end{aligned}$$


The power for each element is

$$\begin{aligned} P_A &= -v_a i_a = -20 \text{ W} & P_B &= v_b i_b = 12 \text{ W} \\ P_C &= v_c i_c = 4 \text{ W} & P_D &= v_d i_d = 4 \text{ W} \end{aligned}$$

Thus, $P_A + P_B + P_C + P_D = 0$.

- P1.45** (a) In Figure P1.28, elements C , D , and E are in parallel.
 (b) In Figure P1.33, no element is in parallel with another element.
 (c) In Figure P1.34, elements C and D are in parallel.

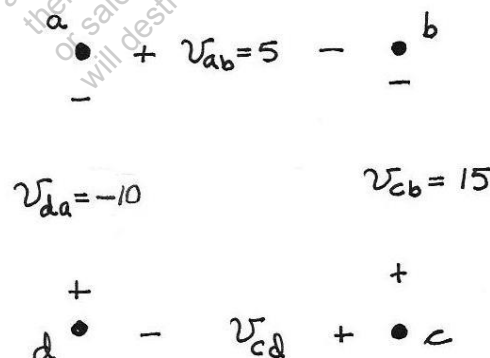P1.46 The points and the voltages specified in the problem statement are:



Applying KVL to the loop $abca$, substituting values and solving, we obtain:


$$\begin{aligned} v_{ab} - v_{cb} - v_{ac} &= 0 \\ 5 - 15 - v_{ac} &= 0 & v_{ac} &= -10 \text{ V} \end{aligned}$$

Similarly, applying KVL to the loop $abcd$, substituting values and solving, we obtain:


$$\begin{aligned} V_{ab} - V_{cb} + V_{cd} + V_{da} &= 0 \\ 5 - 15 + V_{cd} - 10 &= 0 \\ V_{cd} &= 20 \text{ V} \end{aligned}$$

- P1.47** (a) The voltage between any two points of an ideal conductor is zero regardless of the current flowing.
- (b) An ideal voltage source maintains a specified voltage across its terminals.
- (c) An ideal current source maintains a specified current through itself.
- P1.48** Four types of controlled sources and the units for their gain constants are:
1. Voltage-controlled voltage sources. V/V or unitless.
 2. Voltage-controlled current sources. A/V or siemens.
 3. Current-controlled voltage sources. V/A or ohms.
 4. Current-controlled current sources. A/A or unitless.
- P1.49** Provided that the current reference points into the positive voltage reference, the voltage across a resistance equals the current through the resistance times the resistance. On the other hand, if the current reference points into the negative voltage reference, the voltage equals the negative of the product of the current and the resistance.

P1.50*

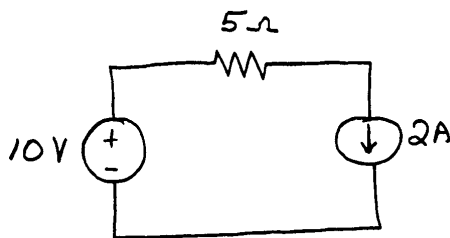


P1.51

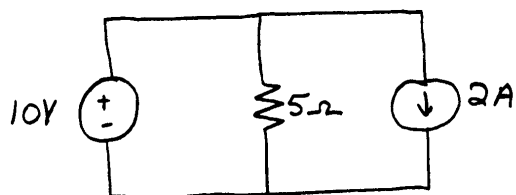


P1.52 The resistance of the copper wire is given by $R_{cu} = \rho_{cu}L/A$, and the resistance of the tungsten wire is $R_W = \rho_W L/A$. Taking the ratios of the respective sides of these equations yields $R_W/R_{cu} = \rho_W/\rho_{cu}$. Solving for R_W and substituting values, we have

$$\begin{aligned} R_W &= R_{cu} \rho_W / \rho_{cu} \\ &= (0.5) \times (5.44 \times 10^{-8}) / (1.72 \times 10^{-8}) \\ &= 1.58 \, \Omega \end{aligned}$$

P1.53

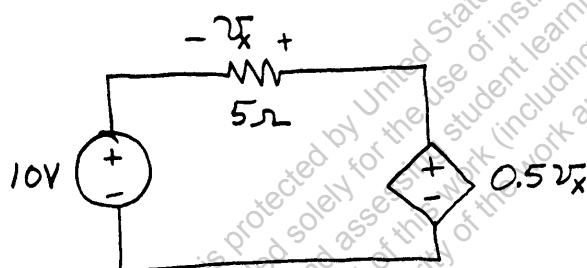

P1.54

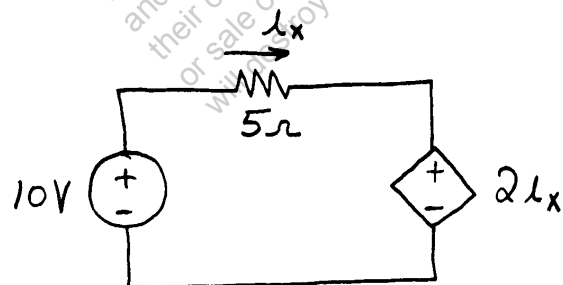

P1.55* $R = \frac{(V_1)^2}{P_1} = \frac{100^2}{100} = 100 \, \Omega$

$$P_2 = \frac{(V_2)^2}{R} = \frac{90^2}{100} = 81 \, \text{W for a 19% reduction in power}$$

P1.56 The power delivered to the resistor is

$$p(t) = v^2(t) / R = 2.5 \exp(-4t)$$

and the energy delivered is

$$w = \int_0^{\infty} p(t) dt = \int_0^{\infty} 2.5 \exp(-4t) dt = \left[\frac{2.5}{-4} \exp(-4t) \right]_0^{\infty} = \frac{2.5}{4} = 0.625 \text{ J}$$

P1.57 The power delivered to the resistor is

$$p(t) = v^2(t) / R = 2.5 \sin^2(2\pi t) = 1.25 - 1.25 \cos(4\pi t)$$

and the energy delivered is

$$w = \int_0^{10} p(t) dt = \int_0^{10} [1.25 - 1.25 \cos(4\pi t)] dt = \left[1.25t - \frac{1.25}{4\pi} \sin(4\pi t) \right]_0^{10} = 12.5 \text{ J}$$

P1.58 Equation 1.10 gives the resistance as

$$R = \frac{\rho L}{A}$$

(a) Thus, if the length of the wire is doubled, the resistance doubles to 1Ω .

(b) If the diameter of the wire is doubled, the cross sectional area A is increased by a factor of four. Thus, the resistance is decreased by a factor of four to 0.125Ω .

P1.59 (a) The voltage across the voltage source is 10 V independent of the current. Thus, we have $v = 10$ which plots as a vertical line in the $v-i$ plane.


(b) The current source has $i = 2$ independent of v , which plots as a horizontal line in the $v-i$ plane.

(c) Ohm's law gives $i = v/5$.

(d) Applying Ohm's law and KVL, we obtain $v = 5i + 10$ which is equivalent to $i = 0.2v - 2$.

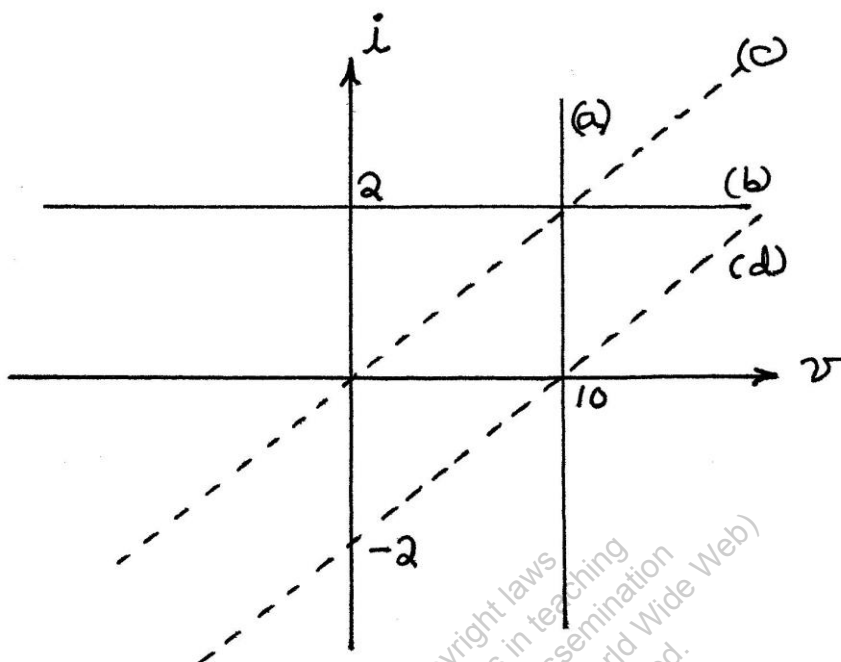(e) Applying KCL and Ohm's law, we obtain $v = 5i + 10$ which is equivalent to $i = 0.2v - 2$.

The plots for all five parts are shown. (Parts d and e have the same plot.)



P1.60* (a) Not contradictory.

(b) A 2-A current source in series with a 3-A current source is contradictory because the currents in series elements must be equal.


(c) Not contradictory.

(d) A 2-A current source in series with an open circuit is contradictory because the current through a short circuit is zero by definition and currents in series elements must be equal.

(e) A 5-V voltage source in parallel with a short circuit is contradictory because the voltages across parallel elements must be equal and the voltage across a short circuit is zero by definition.

P1.61 The power for each element is 20 W. The current source delivers power and the voltage source absorbs it.

P1.62*

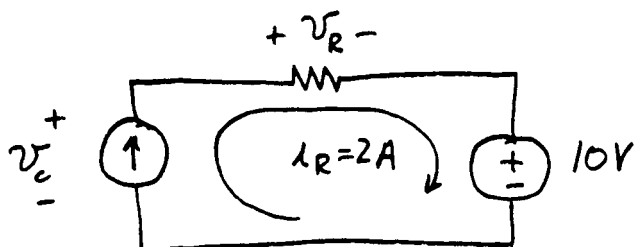

As shown above, the 2 A current circulates clockwise through all three elements in the circuit. Applying KVL, we have

$$v_c = v_R + 10 = 5i_R + 10 = 20 \text{ V}$$

$P_{\text{current-source}} = -v_c i_R = -40 \text{ W}$. Thus, the current source delivers power.

$P_R = (i_R)^2 R = 2^2 \times 5 = 20 \text{ W}$. The resistor absorbs power.

$P_{\text{voltage-source}} = 10 \times i_R = 20 \text{ W}$. The voltage source absorbs power.

P1.63 This is a parallel circuit and the voltage across each element is 10 V positive at the top end. Thus, the current through the resistor is

$$i_R = \frac{10 \text{ V}}{5 \Omega} = 2 \text{ A}$$

Applying KCL, we find that the current through the voltage source is zero. Computing power for each element, we find


$$P_{\text{current-source}} = -20 \text{ W}$$

Thus, the current source delivers power.

$$P_R = (i_R)^2 R = 20 \text{ W}$$

$$P_{\text{voltage-source}} = 0$$

P1.64*

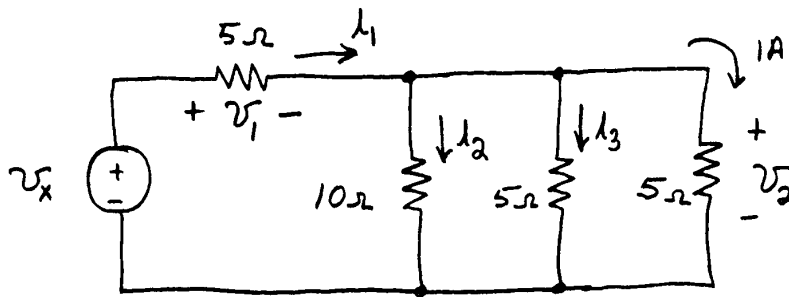


Applying Ohm's law, we have $v_2 = (5\ \Omega) \times (1\ \text{A}) = 5\ \text{V}$. However, v_2 is the voltage across all three resistors that are in parallel. Thus,

$i_3 = \frac{v_2}{5} = 1\ \text{A}$, and $i_2 = \frac{v_2}{10} = 0.5\ \text{A}$. Applying KCL, we have

$i_1 = i_2 + i_3 + 1 = 2.5\ \text{A}$. By Ohm's law: $v_1 = 5i_1 = 12.5\ \text{V}$. Finally using KVL, we have $v_x = v_1 + v_2 = 17.5\ \text{V}$.

P1.65

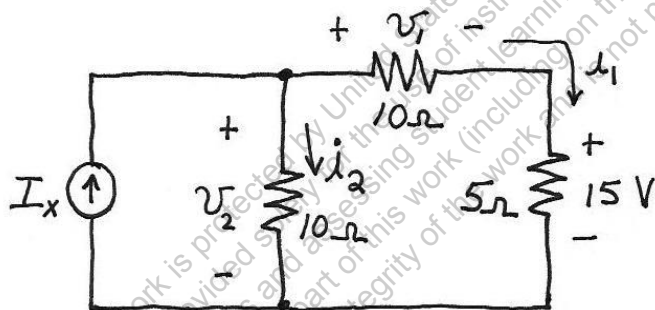

Ohm's law for the $5\text{-}\Omega$ resistor yields: $i_1 = 15/5 = 3\ \text{A}$. Then for the $10\text{-}\Omega$ resistor, we have $v_1 = 10i_1 = 30\ \text{V}$. Using KVL, we have $v_2 = v_1 + 15 = 45\ \text{V}$.


Then applying Ohm's law, we obtain $i_2 = v_2/10 = 4.5\ \text{A}$. Finally applying KCL, we have $I_x = i_1 + i_2 = 7.5\ \text{A}$.

P1.66 (a) The $3\text{-}\Omega$ resistance, the $2\text{-}\Omega$ resistance, and the voltage source V_x are in series.


(b) The $6\text{-}\Omega$ resistance and the $12\text{-}\Omega$ resistance are in parallel.

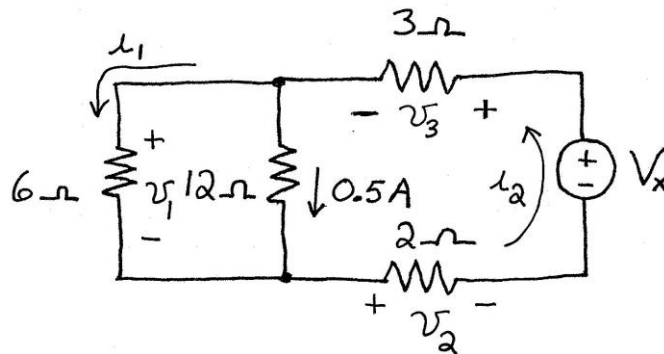(c) Refer to the sketch of the circuit. Applying Ohm's law to the $12\text{-}\Omega$ resistance, we determine that $v_1 = 6\ \text{V}$. Then, applying Ohm's law to the $6\text{-}\Omega$ resistance, we have $i_1 = 1\ \text{A}$. Next, KVL yields $i_2 = 1.5\ \text{A}$. Continuing,

we use Ohm's law to find that $v_2 = 3$ V and $v_3 = 4.5$ V. Finally, applying KVL, we have $V_x = v_3 + v_1 + v_2 = 13.5$ V.




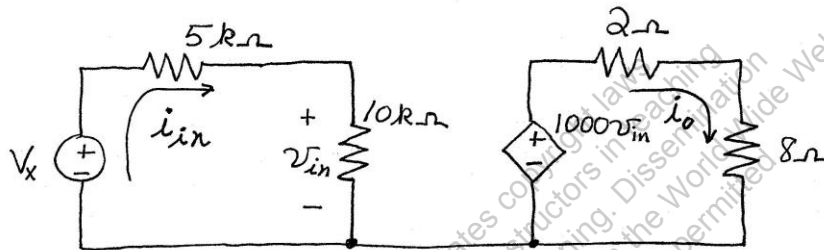P1.67 First, we have $i_o = \sqrt{P_o / 8} = 1$ A.



Applying Ohm's law and KVL to the right-hand loop we have $1000v_{in} = 2i_o + 8i_o$ from which we determine that $v_{in} = 10$ mV. Then, $i_{in} = v_{in} / 10^4 = 1$ μ A, and finally we have $V_x = 5000i_{in} + 10000i_{in} = 15$ mV.

P1.68 (a) No elements are in series.

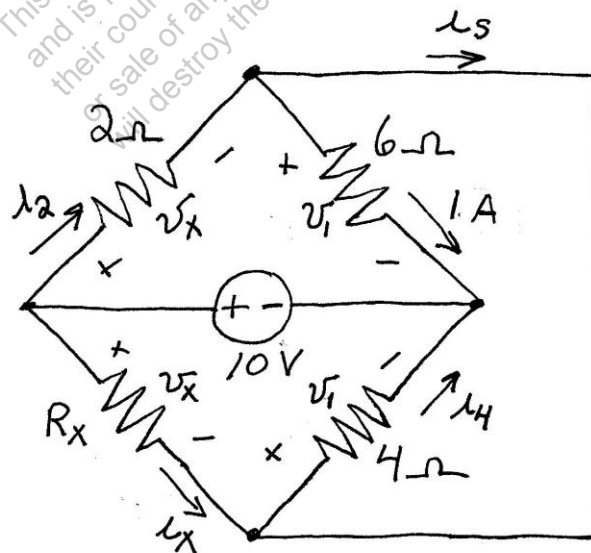

(b) R_x and the $2\text{-}\Omega$ resistor are in parallel. Also, the $6\text{-}\Omega$ resistor and the $4\text{-}\Omega$ resistor are in parallel. Thus, the voltages across the parallel elements are the same as labeled in the figure.

$$\begin{aligned} \text{(c)} \quad v_1 &= 6 \text{ V} \\ i_4 &= v_1 / 4 = 1.5 \text{ A} \\ v_x &= 10 - v_1 = 4 \text{ V} \\ i_2 &= v_x / 2 = 2 \text{ A} \\ i_s &= i_2 - 1 = 1 \text{ A} \\ i_x &= i_4 - i_s = 0.5 \text{ A} \\ R_x &= v_x / i_x = 8 \text{ }\Omega \end{aligned}$$

$$\begin{aligned} \text{P1.69} \quad i_{12} &= v / 12 & i_6 &= v / 6 & i_{12} + i_6 &= v / 12 + v / 6 = 3 \\ v &= 12 \text{ V} & i_{12} &= 1 \text{ A} & i_6 &= 2 \text{ A} \end{aligned}$$

P1.70* (a) Applying KVL, we have $10 = v_x + 5v_x$, which yields $v_x = 10 / 6 = 1.667 \text{ V}$


$$\text{(b)} \quad i_x = v_x / 3 = 0.5556 \text{ A}$$

(c) $P_{\text{voltage-source}} = -10i_x = -5.556 \text{ W}$. (This represents power delivered by the voltage source.)

$$P_R = 3(i_x)^2 = 0.926 \text{ W (absorbed)}$$

$$P_{\text{controlled-source}} = 5v_x i_x = 4.63 \text{ W (absorbed)}$$


P1.71

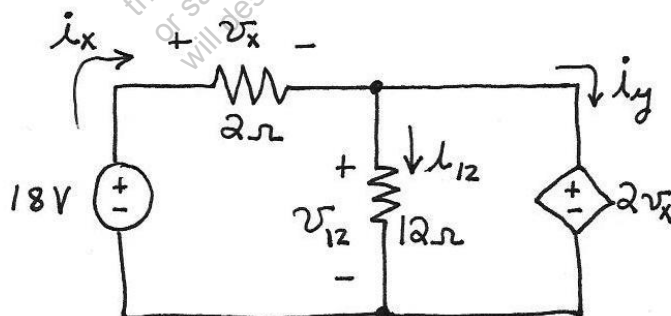


Applying KVL around the periphery of the circuit, we have

$-18 + v_x + 2v_x = 0$, which yields $v_x = 6$ V. Then we have $v_{12} = 2v_x = 12$ V. Using Ohm's law we obtain $i_{12} = v_{12} / 12 = 1$ A and $i_x = v_x / 2 = 3$ A. Then KCL applied to the node at the top of the $12\text{-}\Omega$ resistor gives $i_x = i_{12} + i_y$ which yields $i_y = 2$ A.

- P1.72** Consider the series combination shown below on the left. Because the current for series elements must be the same and the current for the current source is 2 A by definition, the current flowing from a to b is 2 A. Notice that the current is not affected by the 10-V source in series. Thus, the series combination is equivalent to a simple current source as far as anything connected to terminals a and b is concerned.

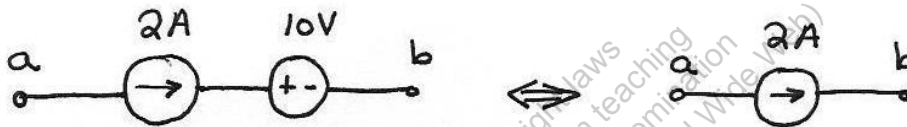


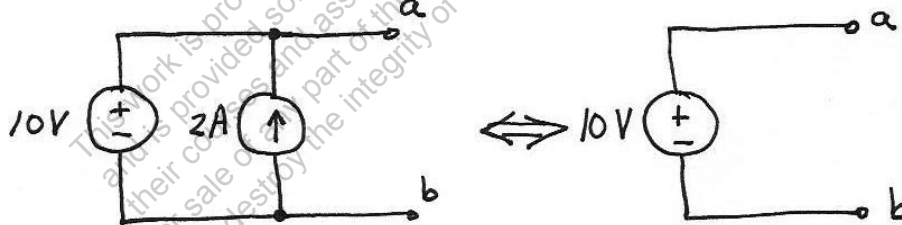- P1.73** Consider the parallel combination shown below. Because the voltage for parallel elements must be the same, the voltage v_{ab} must be 10 V. Notice that v_{ab} is not affected by the current source. Thus, the parallel combination is equivalent to a simple voltage source as far as anything connected to terminals a and b is concerned.



- P1.74**
- (a) $10 = v_1 + v_2$
 - (b) $v_1 = 15i$
 $v_2 = 5i$
 - (c) $10 = 15i + 5i$
 $i = 0.5$ A
 - (d) $P_{\text{voltage-source}} = -10i = -5$ W. (Power delivered by the source.)
 $P_{15} = 15i^2 = 3.75$ W (absorbed)
 $P_5 = 5i^2 = 1.25$ W (absorbed)

P1.75*

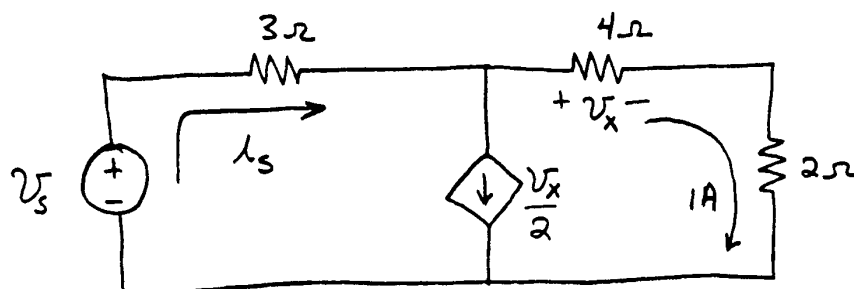

$$v_x = (4 \Omega) \times (1 \text{ A}) = 4 \text{ V}$$

$$i_s = v_x / 2 + 1 = 3 \text{ A}$$

Applying KVL around the outside of the circuit, we have:

$$v_s = 3i_s + 4 + 2 = 15 \text{ V}$$

P1.76 $i_x = -30 \text{ V} / 15 \Omega = -2 \text{ A}$

Applying KCL for the node at the top end of the controlled current source:

$$i_s = i_x / 2 - i_x = -i_x / 2 = 1 \text{ A}$$

The source labeled i_s is an independent current source. The source labeled $i_x / 2$ is a current-controlled current source.

P1.77 Applying Ohm's law and KVL, we have $20 + 10i_x = 5i_x$. Solving, we obtain $i_x = -4 \text{ A}$.

The source labeled 20 V is an independent voltage source. The source labeled $5i_x$ is a current-controlled voltage source.

Practice Test

T1.1 (a) 4; (b) 7; (c) 16; (d) 18; (e) 1; (f) 2; (g) 8; (h) 3; (i) 5; (j) 15; (k) 6; (l) 11;


(m) 13; (n) 9; (o) 14.

T1.2 (a) The current $I_s = 3 \text{ A}$ circulates clockwise through the elements entering the resistance at the negative reference for v_R . Thus, we have $v_R = -I_s R = -6 \text{ V}$.

(b) Because I_s enters the negative reference for V_s , we have $P_V = -V_s I_s = -30$ W. Because the result is negative, the voltage source is delivering energy.

(c) The circuit has three nodes, one on each of the top corners and one along the bottom of the circuit.

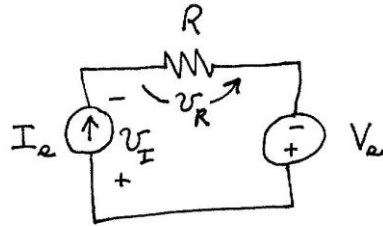(d) First, we must find the voltage v_I across the current source. We choose the reference shown:



Then, going around the circuit counterclockwise, we have $-v_I + V_s + v_R = 0$, which yields $v_I = V_s + v_R = 10 - 6 = 4$ V. Next, the power for the current source is $P_I = I_s v_I = 12$ W. Because the result is positive, the current source is absorbing energy.

Alternatively, we could compute the power delivered to the resistor as $P_R = I_s^2 R = 18$ W. Then, because we must have a total power of zero for the entire circuit, we have $P_I = -P_V - P_R = 30 - 18 = 12$ W.

T1.3

(a) The currents flowing downward through the resistances are v_{ab}/R_1 and v_{ab}/R_2 . Then, the KCL equation for node a (or node b) is

$$I_2 = I_1 + \frac{v_{ab}}{R_1} + \frac{v_{ab}}{R_2}$$

Substituting the values given in the question and solving yields $v_{ab} = -8$ V.

(b) The power for current source I_1 is $P_{I1} = v_{ab} I_1 = -8 \times 3 = -24$ W.

Because the result is negative we know that energy is supplied by this current source.

The power for current source I_2 is $P_{I2} = -v_{ab} I_2 = 8 \times 1 = 8$ W. Because the result is positive, we know that energy is absorbed by this current source.

(c) The power absorbed by R_1 is $P_{R1} = v_{ab}^2 / R_1 = (-8)^2 / 12 = 5.33$ W. The power absorbed by R_2 is $P_{R2} = v_{ab}^2 / R_2 = (-8)^2 / 6 = 10.67$ W.

- T1.4** (a) Applying KVL, we have $-V_s + v_1 + v_2 = 0$. Substituting values given in the problem and solving we find $v_1 = 8 \text{ V}$.
 (b) Then applying Ohm's law, we have $i = v_1 / R_1 = 8 / 4 = 2 \text{ A}$.
 (c) Again applying Ohm's law, we have $R_2 = v_2 / i = 4 / 2 = 2 \Omega$.
- T1.5** Applying KVL, we have $-V_s + v_x = 0$. Thus, $v_x = V_s = 15 \text{ V}$. Next Ohm's law gives $i_x = v_x / R = 15 / 10 = 1.5 \text{ A}$. Finally, KCL yields $i_{sc} = i_x - \alpha v_x = 1.5 - 0.3 \times 15 = -3 \text{ A}$.
- T1.6** Applying Ohm's law to the $40\text{-}\Omega$ resistance, we have $v_4 = 40i_4 = 80 \text{ V}$. Since v_4 is also the voltage across the $20\text{-}\Omega$ and $16\text{-}\Omega$ resistances, we have $i_3 = v_4 / 16 = 80 / 16 = 5 \text{ A}$ and $i_2 = v_4 / 20 = 80 / 20 = 4 \text{ A}$. Then applying KCL to the node joining the resistances, we have $i_1 = i_2 + i_3 + i_4 = 11 \text{ A}$. Then, applying Ohm's law to the $10\text{-}\Omega$ resistance, we have $v_1 = 10i_1 = 110 \text{ V}$. Finally, applying KVL, we have $v_s = v_1 + v_4 = 190 \text{ V}$.

This work is protected by United States Copyright Laws and is provided solely for the use of instructors in teaching their courses and assessing student learning. Dissemination or sale of any part of this work (including on the World Wide Web) will destroy the integrity of the work and is not permitted.