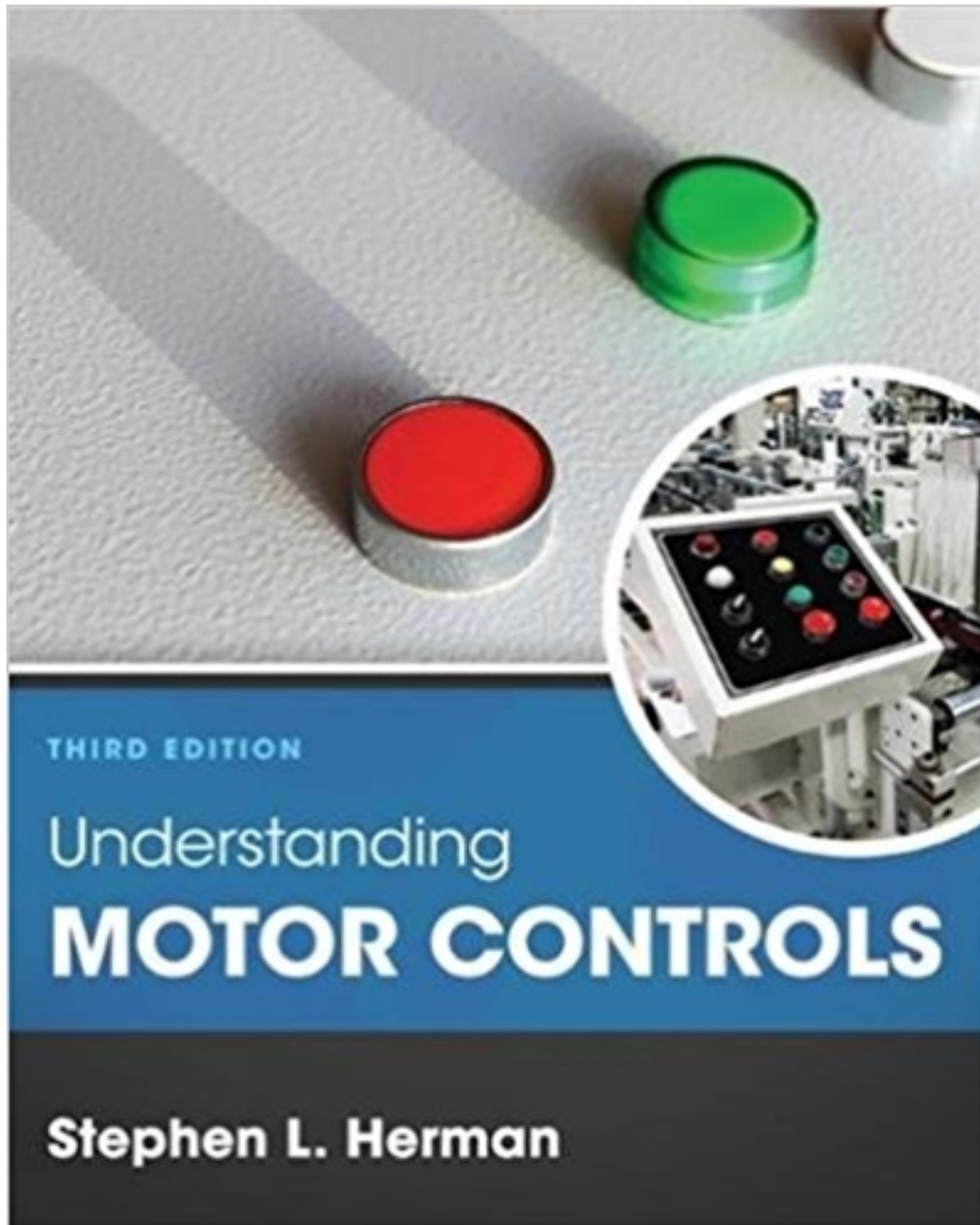


Test Bank for Understanding Motor Controls 3rd Edition by Herman

[CLICK HERE TO ACCESS COMPLETE Test Bank](#)



Test Bank

Name: _____ Class: _____ Date: _____

Chapter 2: Symbols and Schematic Diagrams

1. The double-acting push button has two terminal screws.

- a. True
- b. False

ANSWER: False

POINTS: 1

REFERENCES: Push Buttons

2. Normally open switches are drawn with the movable contact above and touching the stationary contact.

- a. True
- b. False

ANSWER: False

POINTS: 1

REFERENCES: Push Buttons

3. The movable contact of the normally open held closed switch is drawn below the stationary contact.

- a. True
- b. False

ANSWER: True

POINTS: 1

REFERENCES: Push Buttons

4. The symbol for a limit switch illustrates a ball float.

- a. True
- b. False

ANSWER: False

POINTS: 1

REFERENCES: Sensing Devices

5. The flow switch symbol is used for both liquid and air flow switches.

- a. True
- b. False

ANSWER: True

POINTS: 1

REFERENCES: Sensing Devices

6. _____-automatic switches are generally used to select the function of a motor controller either manually or automatically.

ANSWER:
Hand-off
Hand off

POINTS: 1

REFERENCES: Switch Symbols

7. _____ push buttons combine the operation of a selector switch and push button in the same unit.

Name: _____ Class: _____ Date: _____

Chapter 2: Symbols and Schematic Diagrams

ANSWER: Selector

POINTS: 1

REFERENCES: Push Buttons

8. _____ show components in their electrical sequence without regard for physical location.

ANSWER: Schematics

POINTS: 1

REFERENCES: Basic Schematics

9. _____ switches are drawn by adding a wedge to one of the four basic switches.

ANSWER: Limit

POINTS: 1

REFERENCES: Sensing Devices

10. The most common coil symbol used in schematic diagrams is the _____.

ANSWER: circle

POINTS: 1

REFERENCES: Coils

11. What does it mean when components are shown connected by a dashed line in a schematic diagram?

ANSWER: When components are shown connected by a dashed line in a schematic diagram, it indicates that the components are mechanically connected together. If one is pressed, all that are connected by the dashed line are pressed.

POINTS: 1

REFERENCES: Double Acting Push Buttons

12. Name the four basic switch symbols.

ANSWER: There are four basic symbols; normally open (NO), normally closed (NC), normally open held closed (NOHC), and normally closed held open (NCHO).

POINTS: 1

REFERENCES: Switch Symbols

13. What is the function of the contact referred to as a holding, sealing, or maintaining contact?

ANSWER: The function of a holding, sealing, or maintaining contact is to maintain a current path to the coil when the push button returns to its normal open position.

POINTS: 1

REFERENCES: Basic Schematics

14. What are the two basic types of timers?

ANSWER: The two basic types of timers are on delay and off delay.

POINTS: 1

REFERENCES: Timed Contacts

15. Describe the contact symbol.

ANSWER: The contact symbol is two parallel lines connected by wires.

Name: _____ Class: _____ Date: _____

Chapter 2: Symbols and Schematic Diagrams

POINTS: 1

REFERENCES: Contact Symbols